

The basic starter kill relay diagram shown below, breaks continuity of the wire from the ignition switch to the starter motor (or in some cases i.e.; Ford, to another relay), when the alarm is armed and the ignition is turned on. This is the most commonly used application for disabling the starter.

